

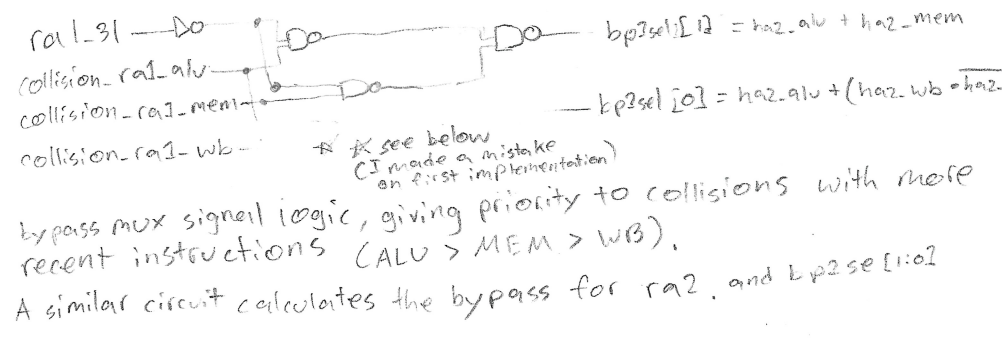


Fully bypassed

 

bypass mux signal logic, giving priority to collisions with more recent instructions (ALU > MEM > WB).
A similar circuit calculates the bypass for ra2, and bp2sel[1:0]




Note *

 

If the collision is with the result of a LD or LDR instruction, we have to wait until it is in the WB stage, so stall if it is in ALU or MEM stage.

The ALU and MEM bypass values are the wdsel[0] muxed values between BSA and alu_out. WB bypass is exactly wdata, which is wdsel[1:0] selected which considers memory output mrd

Partially Bypassed

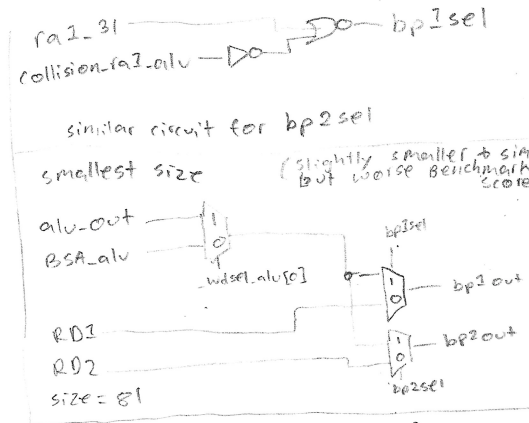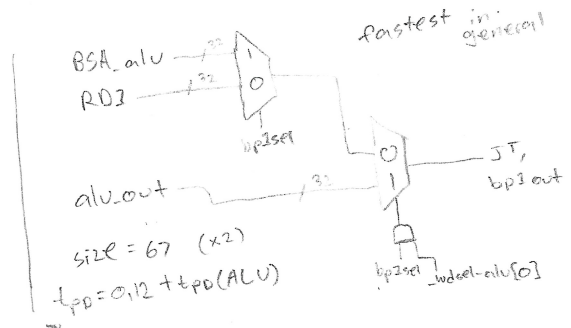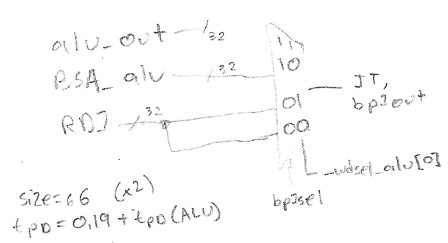


this is the faster implementation, assuming alu_out is the bottleneck input.

In the partially bypassed case, we bypass from ALU stage if there is a non r31 collision with it, as long as it is not a collision with the result of a LD or LDR instruction (as given by wdsel[1]). We stall either way if the collision is with MEM or WB stage. Note: a collision is a matching reg address a hazard is if that match is not r31

Stall was giving me a bunch of problems when the program just started up; of course setting stall to constant 0 gave incorrect program results, but when I added logic to force it to 0 when reset, its value became invalid and ruined everything. I tried a shorter clock period, so the reset signal was stretched over more cycles, and this seemed to allow stall to stay at 0 for long enough until the valid signals had filled the system.

 * Can use raX-31 collision-raX-yyy or reuse signals from bp1sel[1:0] and bp2sel[1:0] computation for size optimization



With this fix, Full bypassing makes much more sense than partial.